

HA

Design Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity HA is
  Port ( a : in  STD_LOGIC; -- Input A
        b : in  STD_LOGIC; -- Input B
        s : out STD_LOGIC; -- Sum output
        c : out STD_LOGIC); -- Carry output
end HA;

architecture Behavioral of HA is
begin

  s <= a xor b;

  c <= a and b;

end Behavioral;
```

Port Name	FPGA Pin
a	R2
b	T1
s	P1
c	L1

FA

Design Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FA is
  Port ( a : in  STD_LOGIC;
        b : in  STD_LOGIC;
        ci : in  STD_LOGIC;
        s : out STD_LOGIC;
        co : out STD_LOGIC);
end FA;

architecture Behavioral of FA is
begin
```

```
s <= a xor b xor ci;
```

```
co <= (a and b) or (ci and (a xor b));
```

```
end Behavioral;
```

Port Name	FPGA Pin
a	R2
b	T1
ci	U1
s	P1
co	L1

RCA

Design Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity FA is
    Port ( a : in  STD_LOGIC;
          b : in  STD_LOGIC;
          ci : in  STD_LOGIC;
          s : out STD_LOGIC;
          co : out STD_LOGIC);
end FA;

architecture Behavioral of FA is
begin
    s <= a xor b xor ci;
    co <= (a and b) or (ci and (a xor b));
end Behavioral;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RCA is
    Port ( a : in  STD_LOGIC_VECTOR (3 downto 0);
          b : in  STD_LOGIC_VECTOR (3 downto 0);
          ci : in  STD_LOGIC;
          s : out STD_LOGIC_VECTOR (3 downto 0);
          co : out STD_LOGIC);
end RCA;
```

```
architecture Structural of RCA is
```

```

component FA is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        ci : in STD_LOGIC;
        s : out STD_LOGIC;
        co : out STD_LOGIC);
end component;

```

```

signal c1, c2, c3 : STD_LOGIC;

```

```

begin

```

```

FA0: FA port map(
  a => a(0),
  b => b(0),
  ci => ci,
  s => s(0),
  co => c1
);

```

```

FA1: FA port map(
  a => a(1),
  b => b(1),
  ci => c1,
  s => s(1),
  co => c2
);

```

```

FA2: FA port map(
  a => a(2),
  b => b(2),
  ci => c2,
  s => s(2),
  co => c3
);

```

```

FA3: FA port map(
  a => a(3),
  b => b(3),
  ci => c3,
  s => s(3),
  co => co
);

```

```

end Structural;

```

a3	R2
a2	T1
a1	U1
a0	W2

b3	R3
b2	T2
b1	T3
b0	V2
ci	V17
s3	L1
s2	P1
s1	N3
s0	P3
co	U16

ALU

Design Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.std_logic_unsigned.all;
```

entity ALU is

```
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (2 downto 0);
          Y : out STD_LOGIC_VECTOR (3 downto 0));
```

end ALU;

architecture Behavioral of ALU is

begin

with S select

```
Y <= A + B when "000",
A - B when "001",
A + 1 when "010",
B + 1 when "011",
A and B when "100",
A or B when "101",
A nand B when "110",
A nor B when "111",
A xor B when others;
```

end Behavioral;

Port Name	FPGA Pin
a3	R2
a2	T1
a1	U1
a0	W2
b3	R3
b2	T2
b1	T3
b0	V2
s2	W16
s1	V16
s0	V17
y3	L1
y2	P1
y1	N3
y0	P3

Mod 16 Counter

Design Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mod16_counter is
  Port (
    clk : in STD_LOGIC;
    dir : in STD_LOGIC;
    reset : in STD_LOGIC;
    count : out STD_LOGIC_VECTOR(3 downto 0)
  );
end mod16_counter;

architecture Behavioral of mod16_counter is
  signal counter : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin

  process(clk, reset)
  begin

```

```

if reset = '1' then
    counter <= "0000";
elsif rising_edge(clk) then
    if dir = '0' then
        -- Count up
        if counter = "1111" then
            counter <= "0000";
        else
            counter <= counter + 1;
        end if;
    else
        -- Count down
        if counter = "0000" then
            counter <= "1111";
        else
            counter <= counter - 1;
        end if;
    end if;
end if;
end process;

count <= counter;

```

end Behavioral;

ADD TO CONSTRAINT FILE

```

set_property PACKAGE_PIN E3 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_IBUF]

```

Port Name	FPGA Pin
clk	V17
dir	R2
reset	T1
c3	L1
c2	P1
c1	N3
c0	P3

USR

Design Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

entity usr1 is
  Port (
    clk : in  STD_LOGIC;
    clk_div : inout std_logic;
    rst : in  STD_LOGIC;
    load: in  STD_LOGIC;
    mode : in  STD_LOGIC_VECTOR(1 downto 0); -- mode selection input
    si : in  STD_LOGIC; -- serial input
    pi : in  STD_LOGIC_VECTOR(3 downto 0); -- parallel input
    so : out STD_LOGIC; -- serial output
    po : out STD_LOGIC_VECTOR(3 downto 0) -- parallel output
  );
end usr1;

architecture Behavioral of usr1 is
  signal shift_reg : STD_LOGIC_VECTOR(3 downto 0);
  signal counter: std_logic_vector(26 downto 0):=( others=>'0');
begin
  process(clk_div, rst,load)
  begin
    if rst = '1' then
      shift_reg <= (others => '0');
    elsif clk_div'event and clk_div= '1' then
      case mode is
        when "00" => -- SISO mode
          shift_reg( 3 downto 1) <= shift_reg(2 downto 0);
          shift_reg(0)<=si;
          so <= shift_reg(3);
        when "01" => -- SIPO mode
          shift_reg( 3 downto 1) <= shift_reg(2 downto 0);
          shift_reg(0)<=si;
          po <= shift_reg;
        when "10" => -- PISO mode
          if(load='0') then
            shift_reg <= pi;
          else
            shift_reg( 3 downto 1) <= shift_reg(2 downto 0);
          end if;
          so <= shift_reg(3);
        when "11" => -- PIPO mode
          po<= pi;
      end case;
    end if;
  end process;
end Behavioral;
```

```

        when others =>
            null;
        end case;
    end if;
end process;

-- so <= shift_reg(3);
-- po <= shift_reg;

process(clk)
begin
    if clk'event and clk = '1' then
        if rst = '1' then
            counter <= (others => '0');
        else
            counter <= counter + '1';
        end if;
    end if;
end process;

```

```
clk_div<= counter(26);
```

```
end Behavioral;
```

Port Name	FPGA Pin
clk	W5
rst	U1
pi3	W17
pi2	W16
pi1	V16
pi0	V17
si	W15
mode1	R2
mode0	T1
load	W2
po3	V19
po2	U19
po1	E19
po0	U16
so	W18
clk_div	L1

FIFO

Design Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity fifo_correct is
  GENERIC
  (
    ADDRESS_WIDTH : integer:=2;---8 bit
    DATA_WIDTH : integer:=4 ---32 bit
  );

  port ( clk : in std_logic;
        clk_div : inout std_logic;
        reset : in std_logic;
        enr : in std_logic; --enable read,should be '0' when not in use.
        enw : in std_logic; --enable write,should be '0' when not in use.
        dataout : out std_logic_vector(DATA_WIDTH-1 downto 0); --output data
        datain : in std_logic_vector (DATA_WIDTH-1 downto 0); --input data
        empty : out std_logic; --set as '1' when the queue is empty
        err : out std_logic;
        full : out std_logic --set as '1' when the queue is full
  );
end fifo_correct;

architecture Behavioral of fifo_correct is

  type memory_type is array (0 to ((2**ADDRESS_WIDTH)-1)) of std_logic_vector(DATA_WIDTH-1 downto 0);

  -----distributed-----
  signal memory : memory_type ;-- :=(others => (others => '0')); --memory for queue.-----
  signal readptr,writeptr : std_logic_vector(ADDRESS_WIDTH-1 downto 0); --read and write pointers.
  signal full0 : std_logic;
  signal empty0 : std_logic;
  signal counter: std_logic_vector(28 downto 0):=( others=>'0');
  begin
    full <= full0;
    empty <= empty0;

    fifo0: process(clk_div,reset,datain,enw,enr)
    begin
      if reset='1' then

        readptr <= (others => '0');
        writeptr <= (others => '0');
        empty0 <='1';
```

```
full0<='0';  
err<='0';
```

```
elsif clk_div'event and clk_div = '1' then  
if enr='1' and full0='0' then  
memory (conv_integer(writeptr)) <= datain ;  
writeptr <= writeptr + '1' ;  
if (writeptr + '1' = readptr) then  
full0<='1';  
empty0<= '0';  
else  
full0<='0';  
empty0<= '1';  
end if ;  
end if ;
```

```
if enr='1' and empty0='0' then
```

```
dataout <= memory (conv_integer(readptr));  
readptr <= readptr + '1' ;  
if (readptr + '1' = writeptr ) then  
empty0<='1';  
full0<='0';  
else  
empty0<='0';  
full0<='1';  
end if ;  
end if ;
```

```
if (empty0='1' and enr='1') or (full0='1' and enr='1') then  
err<='1';  
else  
err<= '0';  
end if ;  
end if;
```

```
end process;
```

```
process(clk)  
begin  
if clk'event and clk= '1' then  
counter<= counter + '1';  
end if;  
end process;
```

```
clk_div<= counter(26);
```

```
end Behavioral;
```

Port Name	FPGA Pin
clk	W5
reset	U1
datain3	W17
datain2	W16
datain1	V16
datain0	V17
enw (enable write)	R2
enr (enable read)	T1
dataout3	V19
dataout2	U19
dataout1	E19
dataout0	U16
empty	L1
full	P1
err	N3
clk_div	P3

Keypad

Design Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity keypad_7seg is
    Port ( clk : in STD_LOGIC;           -- 100 MHz clock
          row : in STD_LOGIC_VECTOR (3 downto 0); -- Rows from keypad (inputs)
          col : out STD_LOGIC_VECTOR (3 downto 0); -- Columns to keypad (outputs)
          seg : out STD_LOGIC_VECTOR (6 downto 0); -- Seven-segment cathodes
          an : out STD_LOGIC_VECTOR (3 downto 0) -- Seven-segment anodes
    );
end keypad_7seg;

architecture Behavioral of keypad_7seg is
    signal col_sel : std_logic_vector(1 downto 0) := "00";
    signal display_digit : std_logic_vector(3 downto 0) := "1111"; -- Latched display value
    signal counter: unsigned(28 downto 0) := (others => '0');

```

```

signal clk_div : std_logic := '0';
begin
  an <= "1110"; -- Enable rightmost digit (AN[0] = 0)

  -- Clock divider process
  process(clk)
  begin
    if clk'event and clk = '1' then
      counter <= counter + 1;
      clk_div <= counter(19);
    end if;
  end process;

  -- Drive columns based on col_sel
  with col_sel select
    col <= "0111" when "00",
           "1011" when "01",
           "1101" when "10",
           "1110" when "11",
           "1111" when others;

  -- Keypad scanning and display latching process
  process(clk_div)
  begin
    if clk_div'event and clk_div = '1' then
      case col_sel is
        when "00" =>
          if row(3) = '0' then display_digit <= "0001"; --1
          elsif row(2) = '0' then display_digit <= "0100"; --4
          elsif row(1) = '0' then display_digit <= "0111"; --7
          elsif row(0) = '0' then display_digit <= "0000"; --0
          end if;
        when "01" =>
          if row(3) = '0' then display_digit <= "0010"; --2
          elsif row(2) = '0' then display_digit <= "0101"; --5
          elsif row(1) = '0' then display_digit <= "1000"; --8
          elsif row(0) = '0' then display_digit <= "1111"; --F
          end if;
        when "10" =>
          if row(3) = '0' then display_digit <= "0011"; --3
          elsif row(2) = '0' then display_digit <= "0110"; --6
          elsif row(1) = '0' then display_digit <= "1001"; --9
          elsif row(0) = '0' then display_digit <= "1110"; --E
          end if;
        when "11" =>
          if row(3) = '0' then display_digit <= "1010"; --A
          elsif row(2) = '0' then display_digit <= "1011"; --B
          elsif row(1) = '0' then display_digit <= "1100"; --C
          elsif row(0) = '0' then display_digit <= "1101"; --D
          end if;
        when others =>
          null;
      end case;
    end if;
  end process;
end;

```

```

-- Cycle col_sel to scan all columns
if col_sel = "11" then
    col_sel <= "00";
else
    col_sel <= std_logic_vector(unsigned(col_sel) + 1);
end if;
end if;
end process;

```

```

-- Seven-segment decoder

```

```

process(display_digit)
begin
    case display_digit is
        when "0000" => seg <= "1000000"; -- 0
        when "0001" => seg <= "1111001"; -- 1
        when "0010" => seg <= "0100100"; -- 2
        when "0011" => seg <= "0110000"; -- 3
        when "0100" => seg <= "0011001"; -- 4
        when "0101" => seg <= "0010010"; -- 5
        when "0110" => seg <= "0000010"; -- 6
        when "0111" => seg <= "1111000"; -- 7
        when "1000" => seg <= "0000000"; -- 8
        when "1001" => seg <= "0010000"; -- 9
        when "1010" => seg <= "0001000"; -- A
        when "1011" => seg <= "0000011"; -- B
        when "1100" => seg <= "1000110"; -- C
        when "1101" => seg <= "0100001"; -- D
        when "1110" => seg <= "0000110"; -- E
        when "1111" => seg <= "0001110"; -- F
        when others => seg <= "1111111"; -- Blank
    end case;
end process;

```

```

end Behavioral;

```